

Task Unit 3: Validation of a Binary to BCD Converter

José Manuel Caballero Sánchez — Master in Microelectronics, University of Seville

1. Objective

The goal of this assignment is to validate the correct operation of a parameterized Binary to BCD converter written in Verilog (N=9) through simulation, fulfilling the following specifications:

1. Correct conversion for N=9.
2. The conversion continues even if the `convierte` pulse goes low before finishing.
3. `rst` is a synchronous high reset active signal that interrupts the ongoing conversion.
4. The input data `IN` can be modified without affecting the current conversion.

2. Validation through Simulation

The description provided by avedillo@us.es was the following:

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 06.11.2018 13:22:39
// Design Name:
// Module Name: unit3_1
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module unit3_1 (clk, rst, convierte, IN, Rcentenas, Rdecenas,
               Runidades, fin, listo);

    parameter N= 9;
    input clk, rst, convierte;
```

```

input [N-1:0] IN;
output reg [3:0] Rcentenas, Rdecenas, Runidades;
output fin, listo;

function integer F1;
    input [31:0] num;
    integer i;

    begin
        i = num;
        for(F1 = 0; i > 0; F1 = F1 + 1)
            i = i >> 1;
    end

endfunction

reg[2:0] ;
reg [N-1:0] RIN;
parameter espera=3'b000, prepara=3'b001, opera1=3'b010, opera2=3'b011, ultimo=3'b100;
reg [2:0] state;
assign listo = (state==espera);
assign fin =(state==ultimo);

always @(posedge clk)

if (rst)
    state<= espera;

else
    case (state)

        espera:

            begin if (convierte == 1)
                state <= prepara;
            else
                state <= espera;
            end

        prepara:

            begin
                Rcentenas <= 0;
                Rdecenas <= 0;
                Runidades <= 0;
                Contador <= N-1;
                RIN <= IN;
                state <= opera1;
            end
    endcase

```

```

opera1:

    begin
        if (Rdecenas >= 5)
            Rdecenas <= Rdecenas +3;

            if (Runidades >=5)
                Runidades <= Runidades + 3;

            if (Rcentenas >=5)
                Rcentenas <= Rcentenas + 3;
                state <= opera2;
            end
        end

opera2:

    begin
        Contador <= Contador -1;
        Rcentenas <= {Rcentenas[2:0], Rdecenas[3]};
        Rdecenas <= {Rdecenas[2:0], Runidades[3]};
        Runidades <= {Runidades[2:0], RIN[N-1]};
        RIN <= RIN << 1;

        if (Contador == 0)
            state <= ultimo;
        else
            state <= opera1;
        end

ultimo:

    state <= espera;

default: state<= espera;

endcase

endmodule

```

Although by inspection we can already identify some issues in the code regarding the required specifications, a dedicated testbench has been created to validate the correct functionality of the design.

```
// ===== TESTBENCH =====
`timescale 1ns/1ps
module tb;
    parameter N = 9;

    reg          clk = 0;
    reg          rst = 0;
    reg          convierte = 0;
    reg  [N-1:0]  IN = 0;
    wire [3:0]    Rcentenas, Rdecenas, Runidades;
    wire          fin, listo;

    unit3_1_fixed #(.N(N)) dut (
        .clk(clk), .rst(rst), .convierte(convierte), .IN(IN),
        .Rcentenas(Rcentenas), .Rdecenas(Rdecenas), .Runidades(Runidades)
        ,
        .fin(fin), .listo(listo)
    );

    // Reloj (100 MHz)
    always #5 clk = ~clk;

    initial begin
        $dumpfile("wave.vcd");
        $dumpvars(0, tb);
    end

    initial begin
        // Reset sincrono
        rst = 1;
        repeat (3) @(posedge clk);
        rst = 0;

        //Requisito 1 y 2 => Prueba 1 y 2
        // PRUEBA 1: IN = 19
        IN = 19;
        convierte = 1;
        @(posedge clk);
        convierte = 0;

        wait (fin == 1);
        @(posedge clk);
        $display("IN=19  -> C:%0d D:%0d U:%0d", Rcentenas, Rdecenas,
            Runidades);

        // PRUEBA 2: IN = 511
        IN = 511;
        convierte = 1;
        @(posedge clk);
        convierte = 0;
    end
endmodule
```

```

wait (fin == 1);
@(posedge clk);
$display("IN=511 -> C:%0d D:%0d U:%0d", Rcentenas, Rdecenas,
        Runidades);

// Requisito 3
// PRUEBA 3: 511 Con rst interrumpiendo
IN = 511;
convierte = 1;
@(posedge clk);
convierte = 0;
repeat (5) @(posedge clk);
rst = 1;
@(posedge clk);
rst = 0;
@(posedge clk);
$display("IN =511 tras reset en medio: C:%0d D:%0d U:%0d",
        Rcentenas, Rdecenas, Runidades);

// Requisito 4
// PRUEBA 4: IN = 19 y luego IN =511
IN = 19;
convierte = 1;
@(posedge clk);
convierte = 0;
repeat (2) @(posedge clk);

IN = 511;
convierte = 1;
@(posedge clk);
convierte = 0;
wait (fin==1);
$display("IN = 19 y cambio IN=511 -> C:%0d D:%0d U:%0d",
        Rcentenas, Rdecenas, Runidades);

$finish;
end
endmodule

```

The obtained result in <https://www.edaplayground.com/> was the following:

```

VCD info: dumpfile wave.vcd opened for output.
IN=19 -> C:0 D:0 U:0
IN=511 -> C:0 D:0 U:1
IN =511 after mid-reset: C=0 D=0 U:1
IN = 19 and change IN=511 -> C:0 D:0 U:0
testbench.sv:82: $finish called at 235000 (1ps)

```

After running the tests, several observations can be made:

1. The converter does not correctly convert either 19 or 511. Both yield incorrect

results (000 and 001), though different — allowing further validation. → Does **not** meet requirement 1.

2. Although the conversion result for 511 is wrong, we can see that when the **convierte** signal is deactivated, the conversion continues and outputs 001. → Meets requirement 2.
3. In Test 3, activating **rst** during an ongoing conversion does not reset the process. It should be noted that, with the current design, a “reset” could seem to occur if the reset occurs too early in the sequence. For this reason, 5 clock cycles were repeated before activating **rst**, ensuring that the system was in an advanced conversion state (**opera1** or **opera2**). Activating **rst** here shows that it does not interrupt the process. If fewer cycles were used (e.g., 2), the output could appear reset but only because the FSM would return to **espera** before starting conversion — inheriting zeros from **prepara**, not due to an actual reset. → Does **not** meet requirement 3.
4. Changing **IN** from 19 to 511 during Test 4 does not affect the ongoing conversion, which still prints the original value of 19 (000). → Meets requirement 4.

3. Correct Description with All Specifications

The corrected design is as follows:

```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 06.11.2018 13:22:39
// Design Name:
// Module Name: unit3_1_fixed
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

module unit3_1_fixed (clk, rst, convierte, IN, Rcentenas, Rdecenas,
    Runidades, fin, listo);

    parameter N = 9;

    // Ports
```

```

input          clk;
input          rst;
input          convierte;
input [N-1:0] IN;

output reg [3:0] Rcentenas;
output reg [3:0] Rdecenas;
output reg [3:0] Runidades;
output        fin;
output        listo;

// Auxiliar function
function integer F1;
  input [31:0] num;
  integer i;
  begin
    i = num;
    for(F1 = 0; i > 0; F1 = F1 + 1)
      i = i >> 1;
  end
endfunction

// Inner registers
reg [F1(N)-1:0] Contador;
reg [N-1:0]     RIN;
reg [2:0]       state;

initial begin
  state      = 3'b000;
  Contador   = 0;
  RIN        = 0;
  Rcentenas  = 0;
  Rdecenas   = 0;
  Runidades  = 0;
end

// States
parameter espera = 3'b000,
             prepara = 3'b001,
             opera1  = 3'b010,
             opera2  = 3'b011,
             ultimo  = 3'b100;

// Status signals
assign listo = (state == espera);
assign fin   = (state == ultimo);

// Main
always @(posedge clk) begin

  if (rst) begin

```

```

state      <= espera;
Rcentenas <= 0;
Rdecenas  <= 0;
Runidades <= 0;
Contador  <= 0;
RIN       <= 0;

end else begin
  case (state)

    espera: begin

      if (convierte == 1)
        state <= prepara;
      else
        state <= espera;
      end

    prepara: begin
      Rcentenas <= 0;
      Rdecenas  <= 0;
      Runidades <= 0;
      RIN       <= IN;
      Contador  <= N-1;
      state     <= opera1;
    end

    opera1: begin
      if (Rdecenas >= 5) Rdecenas <= Rdecenas + 3;
      if (Runidades >= 5) Runidades <= Runidades + 3;
      if (Rcentenas >= 5) Rcentenas <= Rcentenas + 3;
      state <= opera2;
    end

    opera2: begin
      Contador <= Contador - 1;
      Rcentenas <= {Rcentenas[2:0], Rdecenas[3]};
      Rdecenas  <= {Rdecenas [2:0], Runidades[3]};
      Runidades <= {Runidades[2:0], RIN[N-1]};
      RIN       <= RIN << 1;

      if (Contador == 0)
        state <= ultimo;
      else
        state <= opera1;
      end

    ultimo: begin
      state <= espera;
    end
  end case
end

```



```

        default: begin
            state <= espera;
        end

    endcase
end

end

endmodule

```

- First, an **adaptation and standardization of the original code** was performed to improve readability and adhere to Verilog HDL best coding practices.
- The module structure was reorganized, clearly separating *port declarations*, *parameters*, *internal signals*, *auxiliary functions*, and the *main sequential block*.
- A consistent format was applied for indentation, spacing, and comments, improving clarity and maintainability.
- Explanatory comments were added, and assignments were rewritten in an ordered and uniform way.
- An **initial** block was added to ensure all signals start from a defined value at the start of the simulation, avoiding undefined (X) states.

With all these improvements, a more coherent and readable version of the original design — named **unit3_1_fixed** — was obtained. In addition, several functional corrections were introduced:

1. **Dynamic counter width:** The original version used a fixed 3-bit counter, which caused overflow errors. The new version uses the F1 function to automatically calculate the required bit width ($[F1(N)-1:0]$), ensuring the correct behavior for any N.
2. **Controlled register initialization:** An **initial** block sets all registers to zero at startup, preventing undefined states during the first cycles.
3. **Signal cleanup during the waiting state:** In the original design, after returning to **espera** (the waiting state) following a reset or the end of a conversion, some output registers retained residual values from the previous operation. In the updated version, these signals are cleared **when rst is activated** and reinitialized in **prepara** at the start of each new conversion, ensuring consistent outputs before the next cycle begins.
4. **Improved synchronous reset:** The **rst** signal now performs a complete synchronous reset of the FSM and internal registers, **forcing a return to espera upon activation** with outputs and counters set to zero. This guarantees that every new conversion starts from a fully defined and stable condition.

5. **Main logical behavior preserved:** The *double dabble* conversion algorithm in the `opera1` and `opera2` states was kept identical to maintain functional equivalence.
6. **Minor style and consistency corrections:** Conditions and assignments were compacted when convenient for better readability while preserving semantics.

With these modifications, the new design **successfully meets all the required specifications**. In particular, improvements 1, 3, and 4 fix the main issues — the first solves incorrect conversion (requirement 1), while 3 and 4 address the lack of proper reset handling (requirement 3).

4. Results

For the improved design, the same **testbench** was used, and the result obtained in <https://www.edaplayground.com/> was:

```
VCD info: dumpfile wave.vcd opened for output.  
IN=19 -> C:0 D:1 U:9  
IN=511 -> C:5 D:1 U:1  
IN =511 after mid-reset: C=0 D=0 U=0  
IN = 19 and change IN=511 -> C:0 D:1 U:9  
testbench.sv:82: $finish called at 665000 (1ps)
```

We can observe that the conversion is now correct for both 19 and 511, even when `convierte` is deactivated; the reset correctly clears all registers, and changing `IN` during an active conversion does not affect the result, as expected.

Finally, the generated waveform file confirms the correct evolution of the states and output signals:

 


Figure 1: Waveform file wave.vcd generated after simulation